

# THE BUILDING BLOCKS: BOOLEAN LOGIC AND GATES



<https://xkcd.com/356/>



# LEARNING OBJECTIVES

- Simple binary functions
  - one and two inputs with a single output
- Boolean values = binary values
  - Boolean logic
- Truth tables
- Transistors as switches
- Building boolean/binary functions with transistors
- Logic gates



# HOW DO WE MANIPULATE NUMBERS IN CIRCUITS?

- We have seen how it is possible to encode properties about the world (including text, sound and images) into numbers
- We have seen how to encode numbers into binary, either integers or floating point
  - remember the "Why Binary" slide in Lecture 2
- How do we manipulate those numbers? i.e. perform operations on them?
- We are going to build circuits to provide the operations we want to perform on those numbers
  - the presence or absence of a voltage on a wire will indicate 1 or 0
  - we will have many wires e.g. 8 to carry an 8-bit number and pass the values through a circuit which produces an 8-bit answer coming out on 8 wires



# STILL CHAPTER 4



# SIMPLEST EXAMPLE - ONE INPUT FUNCTIONS

- All possible functions which take a value of either 0 or 1 and transform those values
- 1 input (A in this case) can take on  $2^1$  or 2 different values, so we have two rows in our table and  $2^2$  or 4 different functions
- These functions are known as the "zero", "identity", "not" and "one" functions
- The "zero", "identity" and "one" functions are trivial to implement in a circuit

A	Output
0	0
1	0

A	Output
0	0
1	1

A	Output
0	1
1	0

A	Output
0	1
1	1



# TWO INPUT FUNCTIONS

- What do we get if we allow two inputs A and B?
- We have  $2^2$  rows and  $2^4$  or 16 different functions
- The coloured functions are special

A	B	Output
0	0	0
0	1	0
1	0	0
1	1	0

A	B	Output
0	0	1
0	1	0
1	0	0
1	1	0

A	B	Output
0	0	0
0	1	1
1	0	0
1	1	0

A	B	Output
0	0	1
0	1	1
1	0	0
1	1	0

A	B	Output
0	0	0
0	1	0
1	0	1
1	1	0

A	B	Output
0	0	1
0	1	0
1	0	1
1	1	0

A	B	Output
0	0	0
0	1	1
1	0	1
1	1	0

A	B	Output
0	0	1
0	1	1
1	0	1
1	1	0

A	B	Output
0	0	0
0	1	0
1	0	0
1	1	1

A	B	Output
0	0	1
0	1	0
1	0	0
1	1	1

A	B	Output
0	0	0
0	1	1
1	0	0
1	1	1

A	B	Output
0	0	1
0	1	1
1	0	0
1	1	1

A	B	Output
0	0	0
0	1	0
1	0	1
1	1	1

A	B	Output
0	0	1
0	1	0
1	0	1
1	1	1

A	B	Output
0	0	0
0	1	1
1	0	1
1	1	1

A	B	Output
0	0	1
0	1	1
1	0	1
1	1	1



# ARE THEY REALLY NUMBERS?

- The two values 1 and 0 are completely arbitrary - how we interpret them depends on what we are doing
- **Boolean logic** is used for manipulating true/false expressions
- Binary 1/0 maps to true/false of Boolean logic
- Boolean expressions are true or false:  $x \leq 35$ ,  $a = 12$
- Boolean operators:  $(0 \leq x)$  AND  $(x \leq 35)$ ,  $(a = 12)$  OR  $(a = 13)$ , NOT  $(a = 12)$

$$(0 \leq x) \bullet (x \leq 35), (a = 12) + (a = 13), \sim(a = 12)$$

So AND can be represented as  $\bullet$  (we will see that sometimes the  $\bullet$  is not shown), OR can be represented as  $+$ , NOT can be represented as  $\sim$ .  
NOT is also represented as a bar e.g.  $\bar{a}$



# TRUTH TABLE - AND

- **Truth tables** lay out true/false values for Boolean expressions, for each possible true/false input

**FIGURE 4.14**

Inputs: a	Inputs: b	Output a AND b (also written a . b) or just ab
False	False	False
False	True	False
True	False	False
True	True	True

Truth table for the AND operation



# TRUTH TABLE - OR

**FIGURE 4.15**

Inputs: a	Inputs: b	Output a OR b (also written $a + b$ )
False	False	False
False	True	True
True	False	True
True	True	True

Truth table for the OR operation



# TRUTH TABLE - NOT

FIGURE 4.16


Inputs: a	Output NOT a (also written $\bar{a}$ , or $\sim a$ )
False	True
True	False

Truth table for the NOT operation



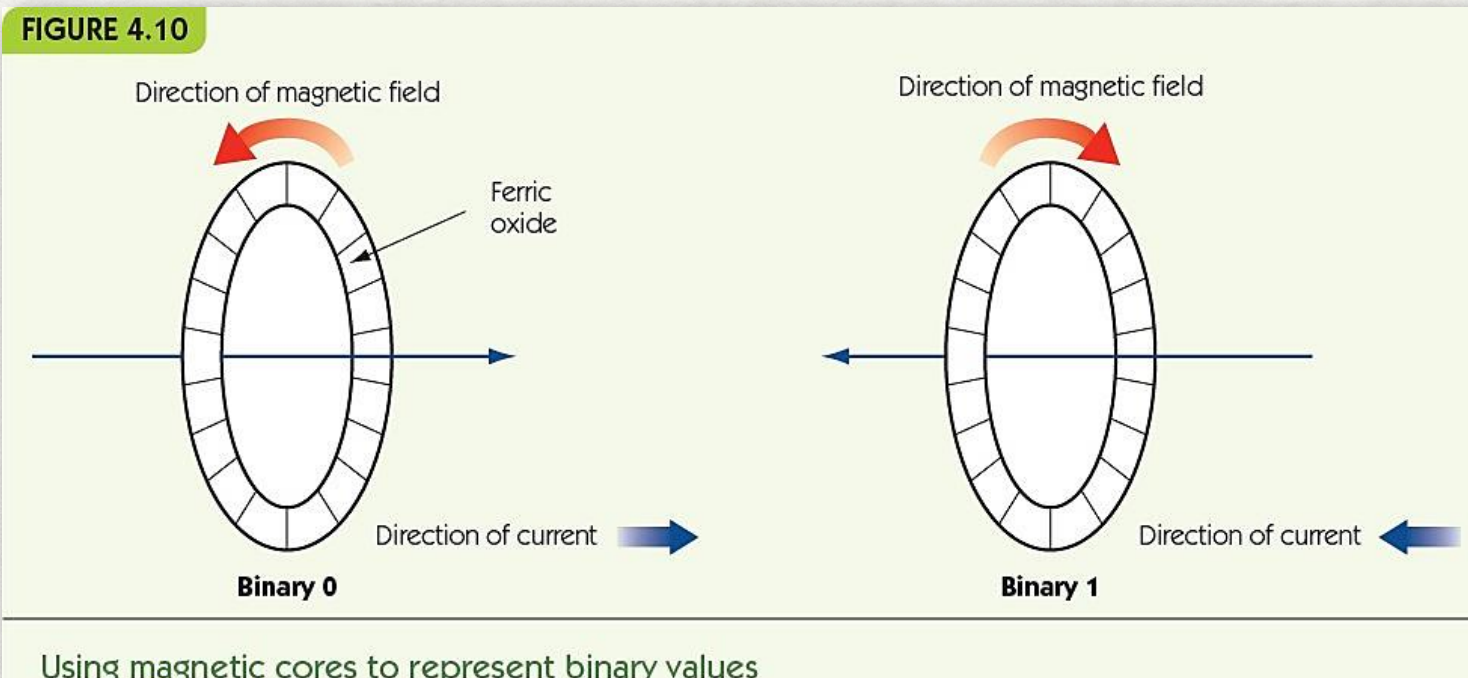
# THE HARDWARE

- We need to be able to represent our two values and turn values on and off
- The ways of representing the two values have changed over time
- Computers use binary because “bistable” systems are reliable
  - Current on/off
  - Magnetic field left/right





# SIMPLE SWITCH

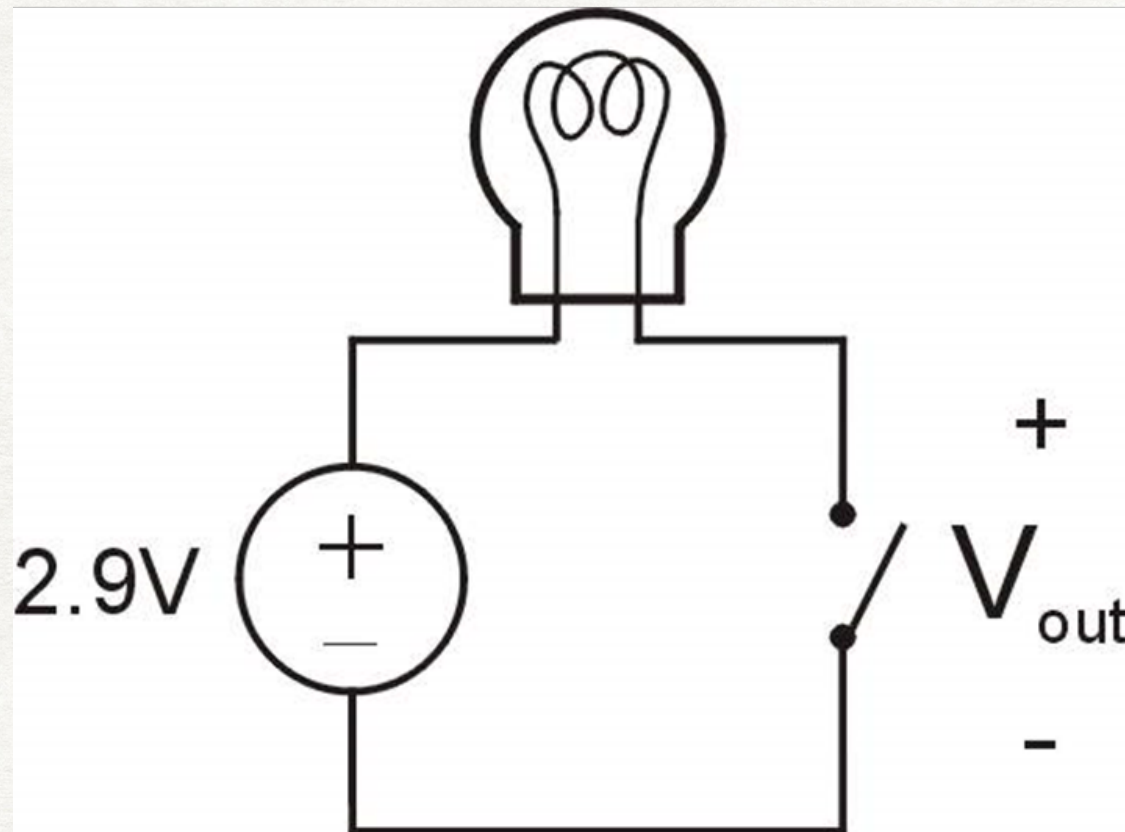

Switch **open**:

- No current through circuit
- Light is **off**

Switch **closed**:

- Short circuit across switch
- Current flows
- Light is **on**


*Switch-based circuits* can easily represent two states:  
on/off, open/closed, voltage/no voltage.



# TRANSISTORS

- Transistors
  - Solid-state switches
  - Change on/off when given power on control line
  - Extremely small (billions per chip)
  - Enable computers that work with **gigabytes** of data

FIGURE 4.12

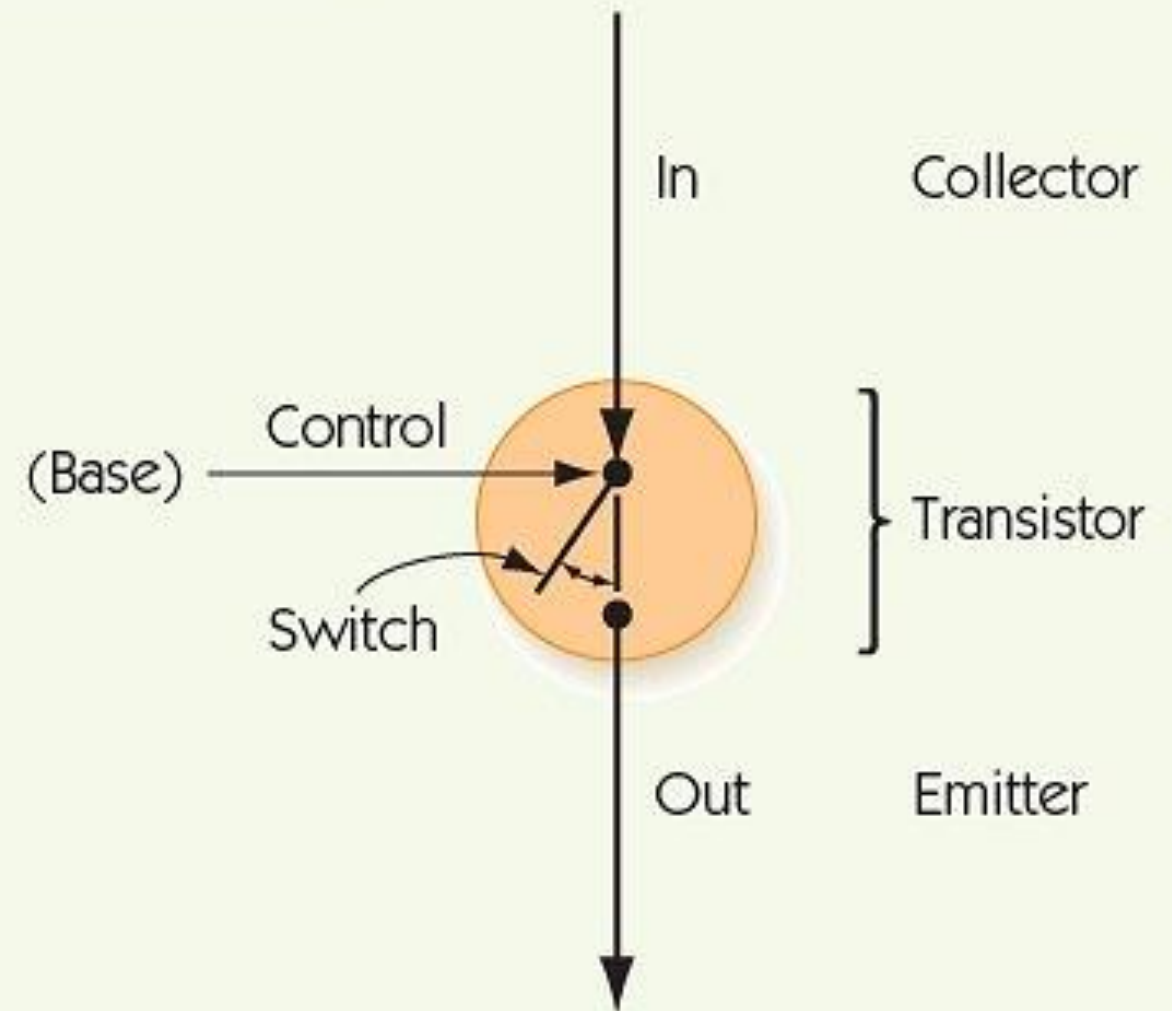

Simplified model of a transistor




# TRANSISTORS

- How do they work as switches? <https://www.youtube.com/watch?v=stM8dgcY1CA> start at 4:50 (not examinable but useful to have an overview of how transistors work)
- Great old video - <https://www.youtube.com/watch?v=V9xUQWo4vN0> (not necessary for this course)



# WHAT A COMPUTER LOOKS LIKE

FIGURE 4.11

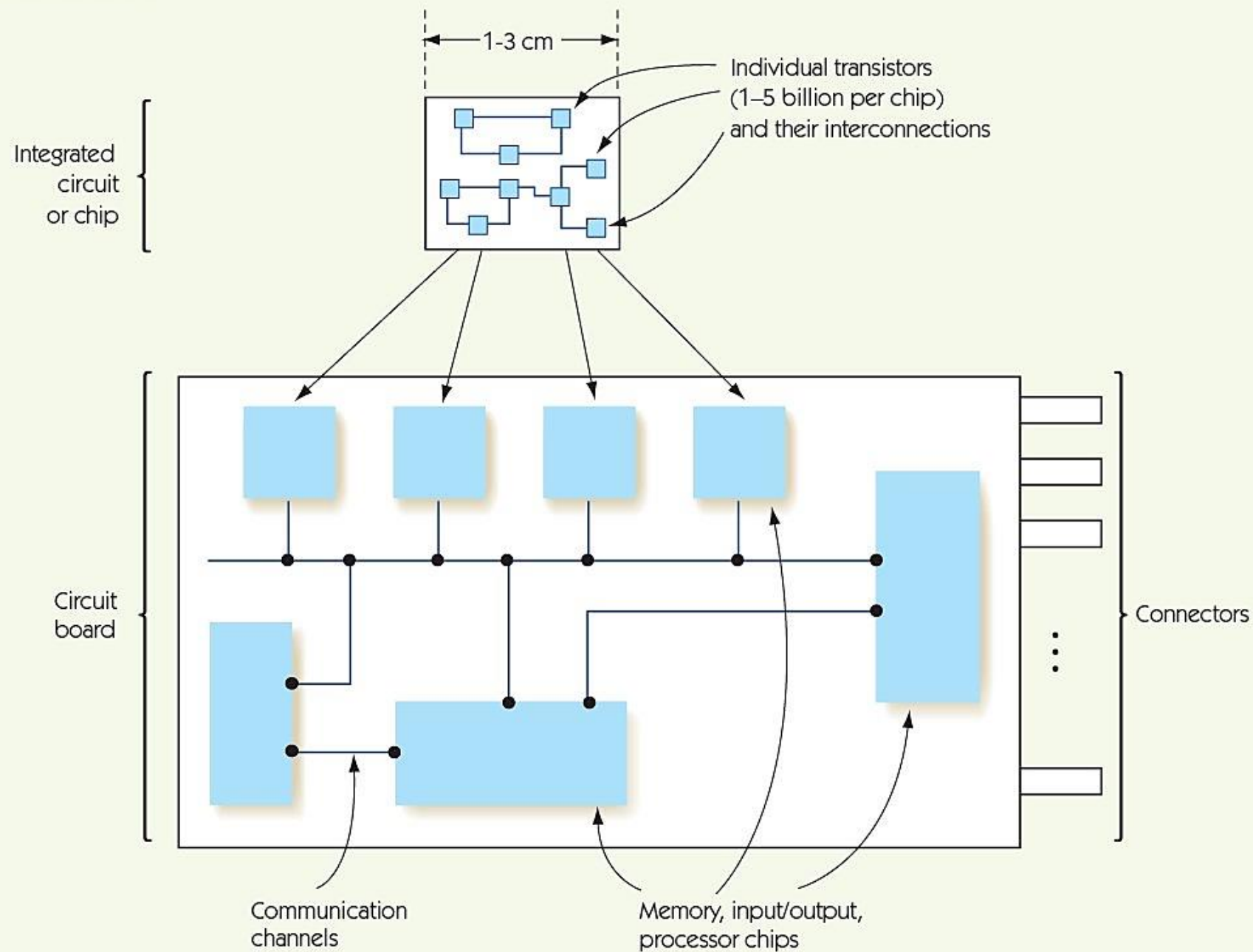

Relationships among transistors, chips, and circuit boards



# PROCESSORS AND TRANSISTORS


- Microprocessors contain millions of transistors
  - Intel® Xeon Phi™ coprocessor 5110P(2012): 5 billion
  - Spark M7 (2015): 10 billion
- Logically, each transistor acts as a switch
- Combined to implement logic functions
  - AND, OR, NOT - these are **functionally complete**, we can use them to create any logic function (see slide "Two Input Functions")
- Combined to build higher-level structures
  - Adder, multiplexer, decoder, register, ...




# GATES

- **Gate:** an electronic device that operates on inputs to produce outputs
- Each gate corresponds to a Boolean operator


**FIGURE 4.17**

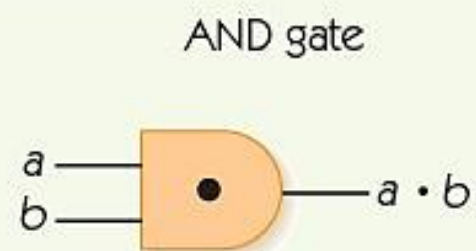

$a$	$b$	$a \cdot b$
0	0	0
0	1	0
1	0	0
1	1	1

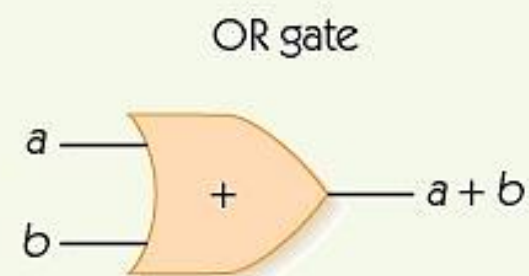

$a$	$b$	$a + b$
0	0	0
0	1	1
1	0	1
1	1	1

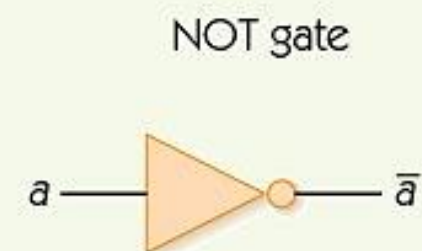

$a$	$\bar{a}$
0	1
1	0


The three basic gates and their symbols



# NOT

- Gates are built from transistors
- NOT gate: 1 transistor
- AND gate: 3 transistors
- OR gate: 3 transistors
- NAND and NOR: 2 transistors
- Transistors can be in series or parallel

**FIGURE 4.18**

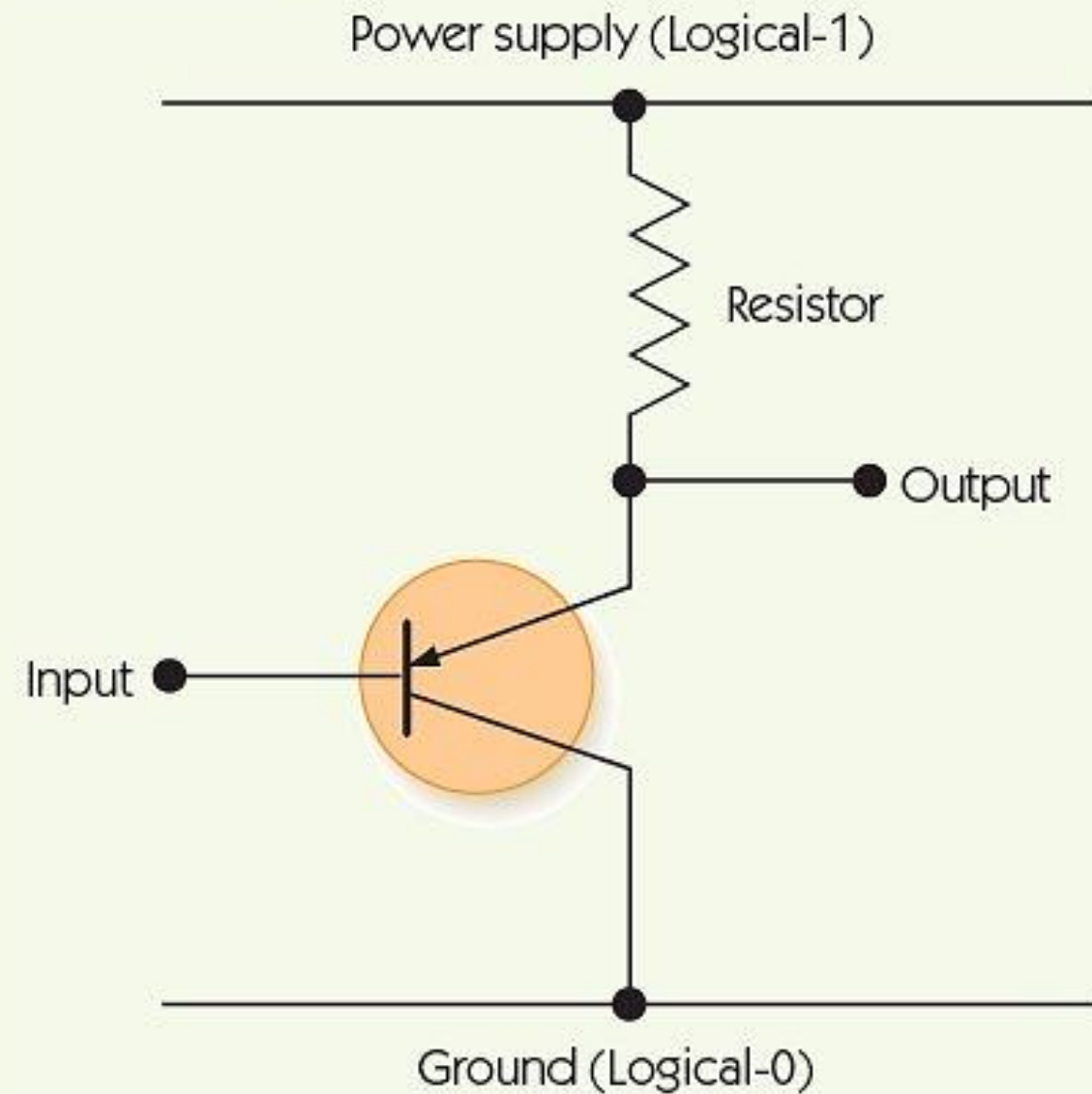


Construction of a NOT gate



# NAND AND AND

FIGURE 4.19

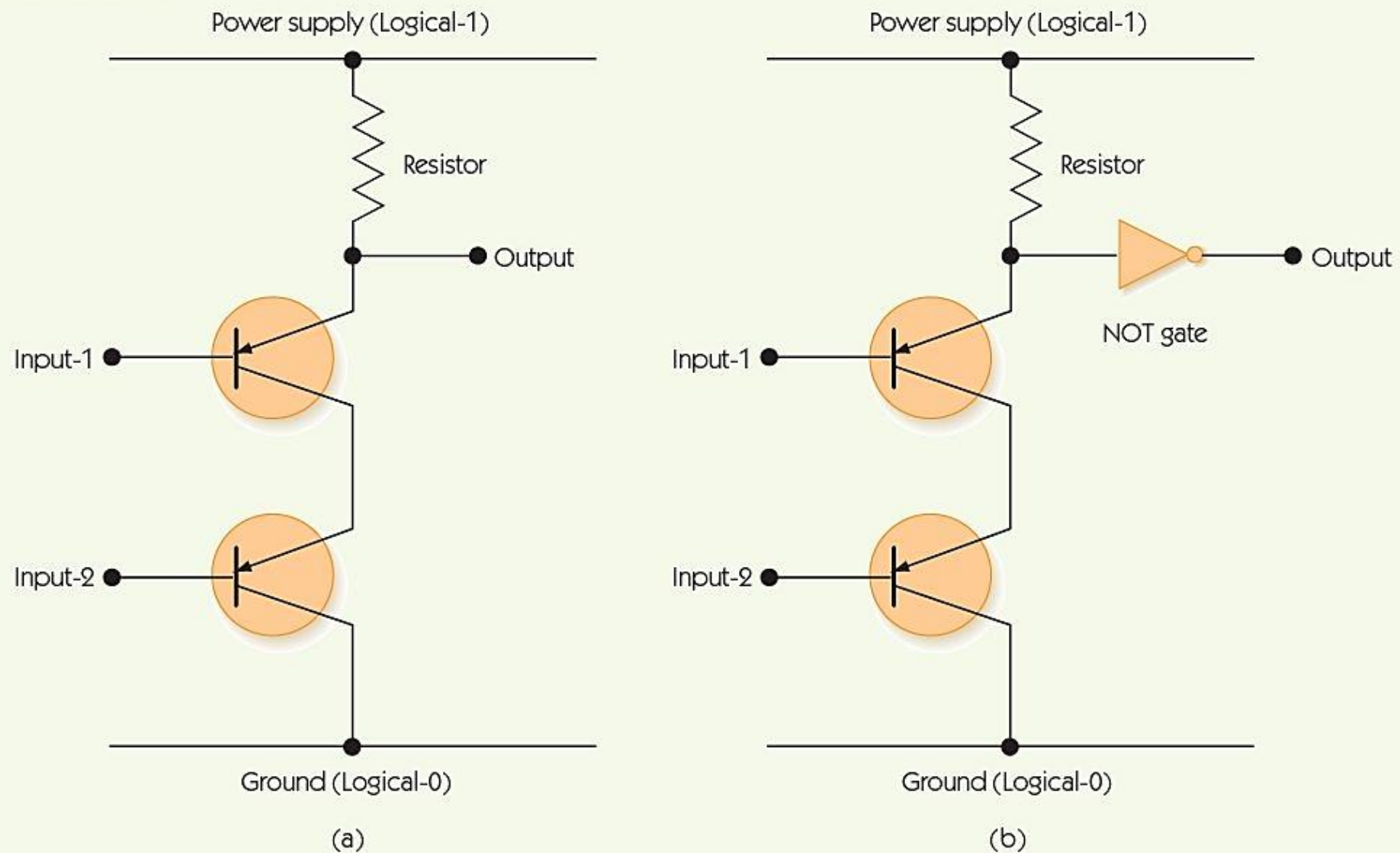

Construction of NAND and AND gates

(a) A two-transistor NAND gate

(b) A three-transistor AND gate



# BUILD SOME OF THE TWO INPUT FUNCTIONS




A	B	Output
0	0	1
0	1	1
1	0	1
1	1	0

NAND

A	B	Output
0	0	0
0	1	0
1	0	0
1	1	1

AND


out of the 16

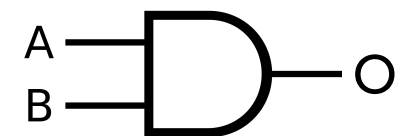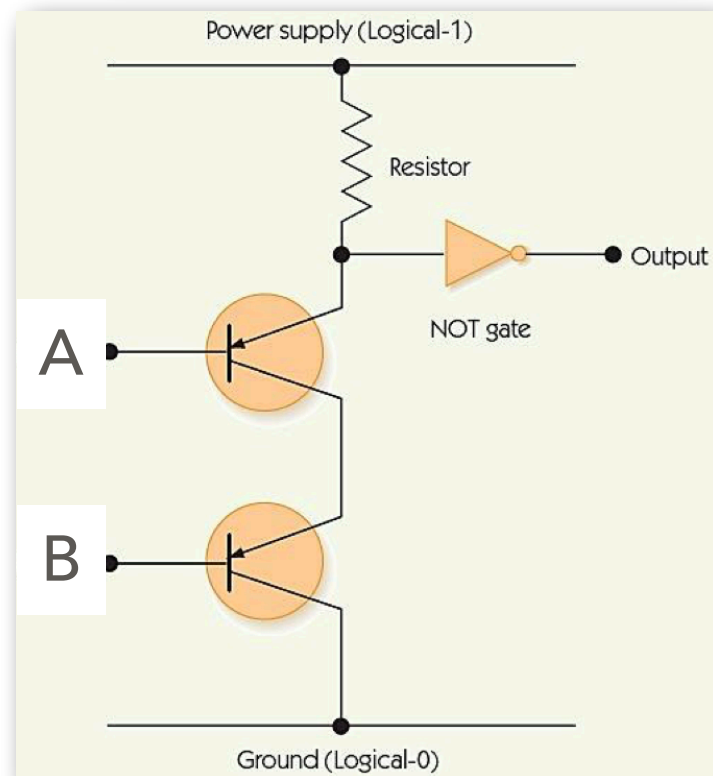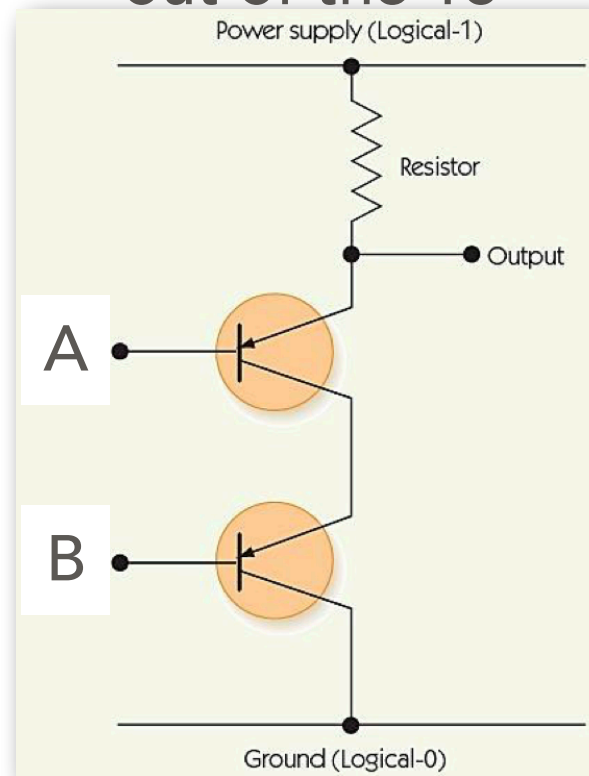



# NOR AND OR

FIGURE 4.20

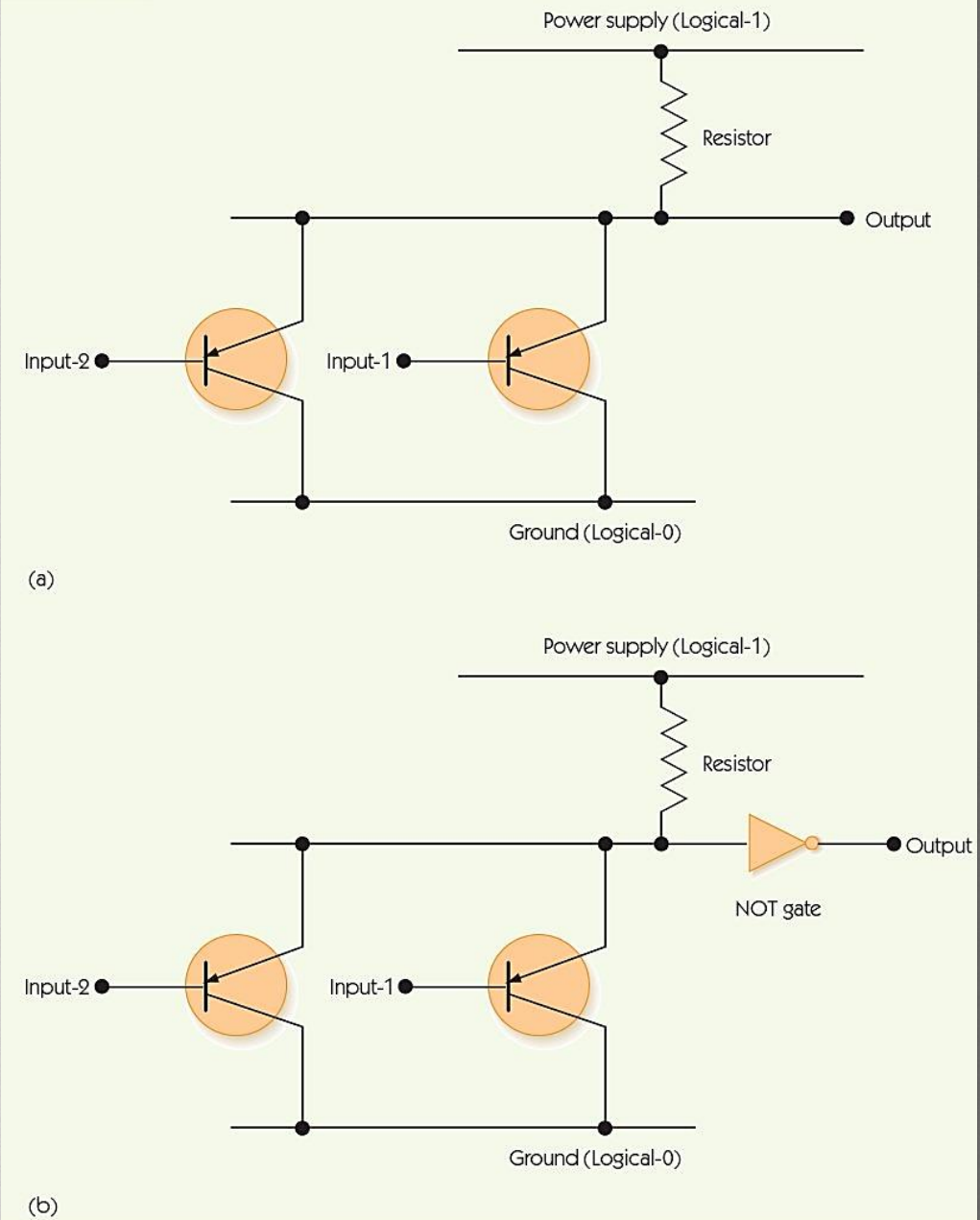

Construction of NOR and OR gates

(a) A two-transistor NOR gate

(b) A three-transistor OR gate





# BUILD SOME OF THE TWO INPUT FUNCTIONS

out of the 16



A	B	Output
0	0	1
0	1	0
1	0	0
1	1	0

NOR

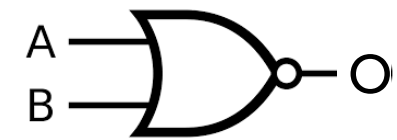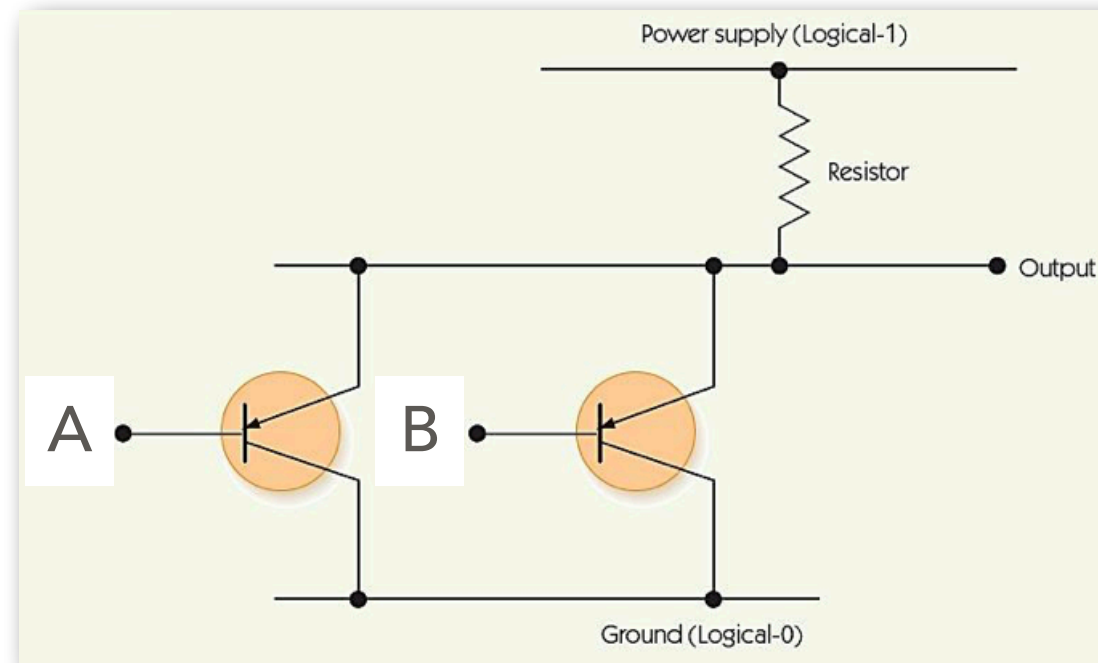

A	B	Output
0	0	0
0	1	1
1	0	1
1	1	1

OR

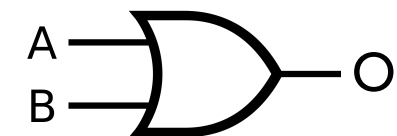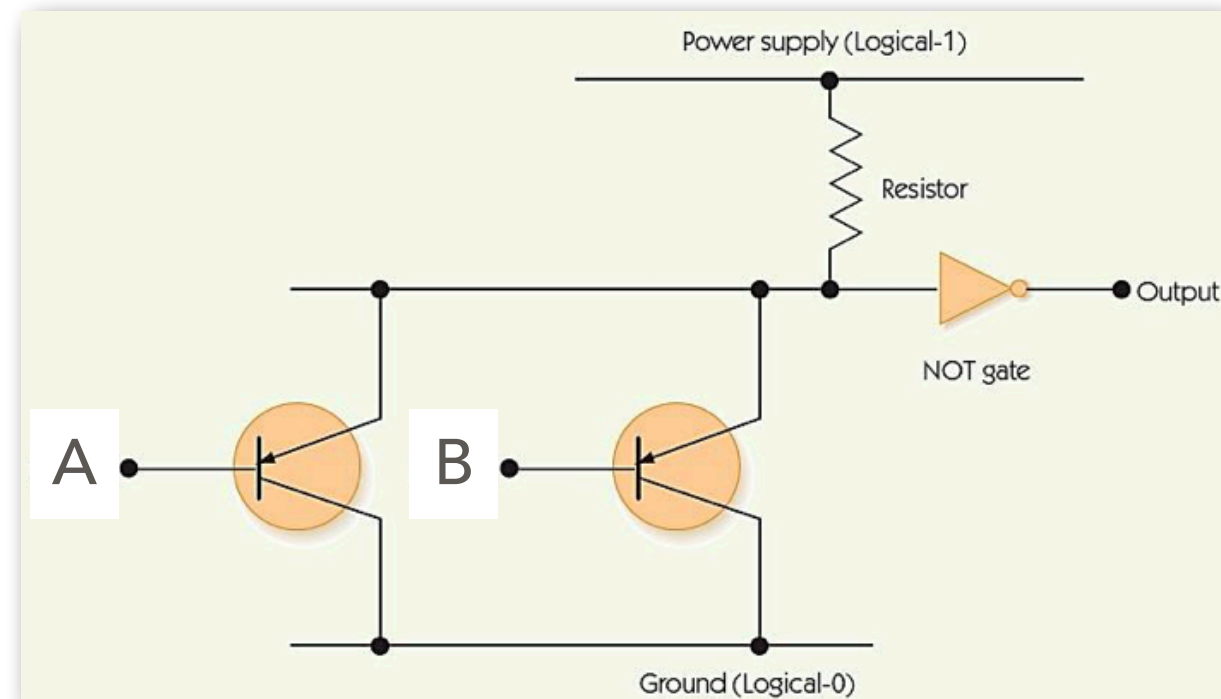



# COMBINATIONAL CIRCUIT

- **Circuit:** has input wires, contains gates connected by wires, and has output wires
- Outputs depend *only* on current inputs: no state

**FIGURE 4.21**

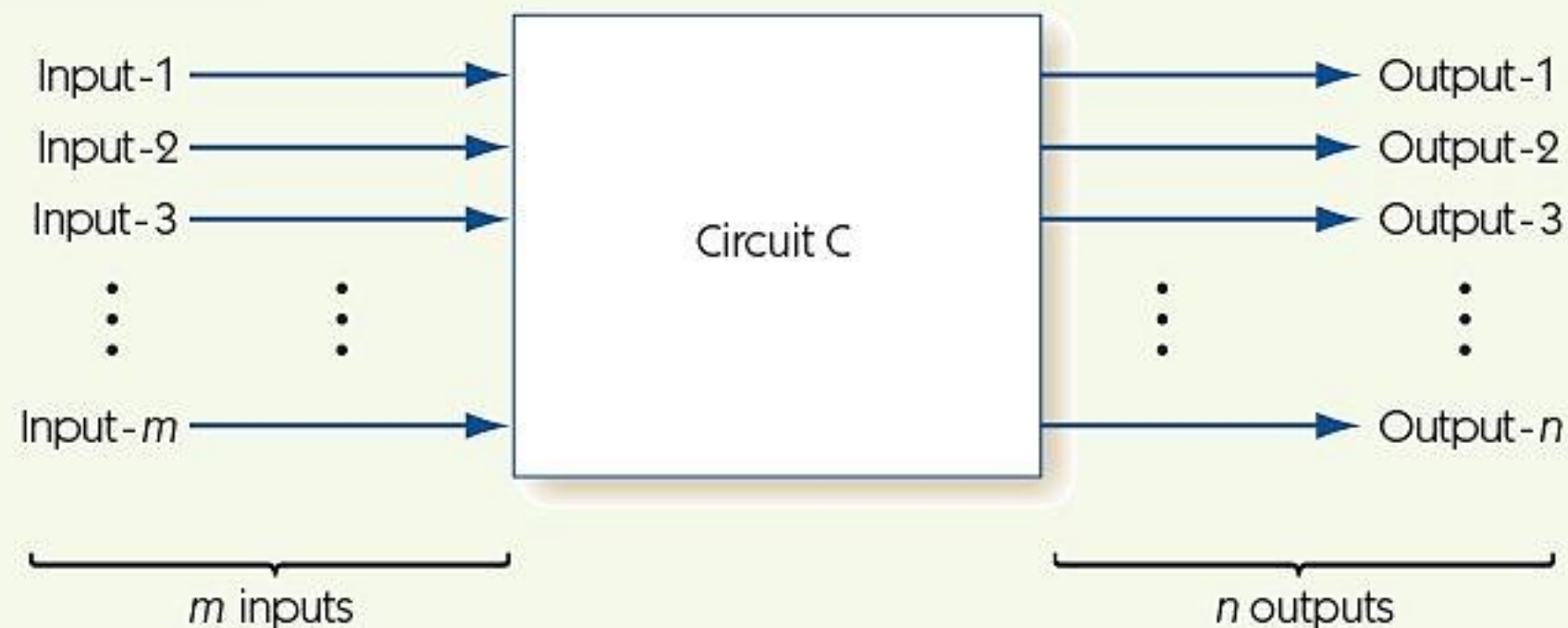


Diagram of a typical computer circuit



# ABSTRACTION

- From now on we don't draw the transistors in our circuits
- The basic elements will be the logic gates, NOT, AND and OR