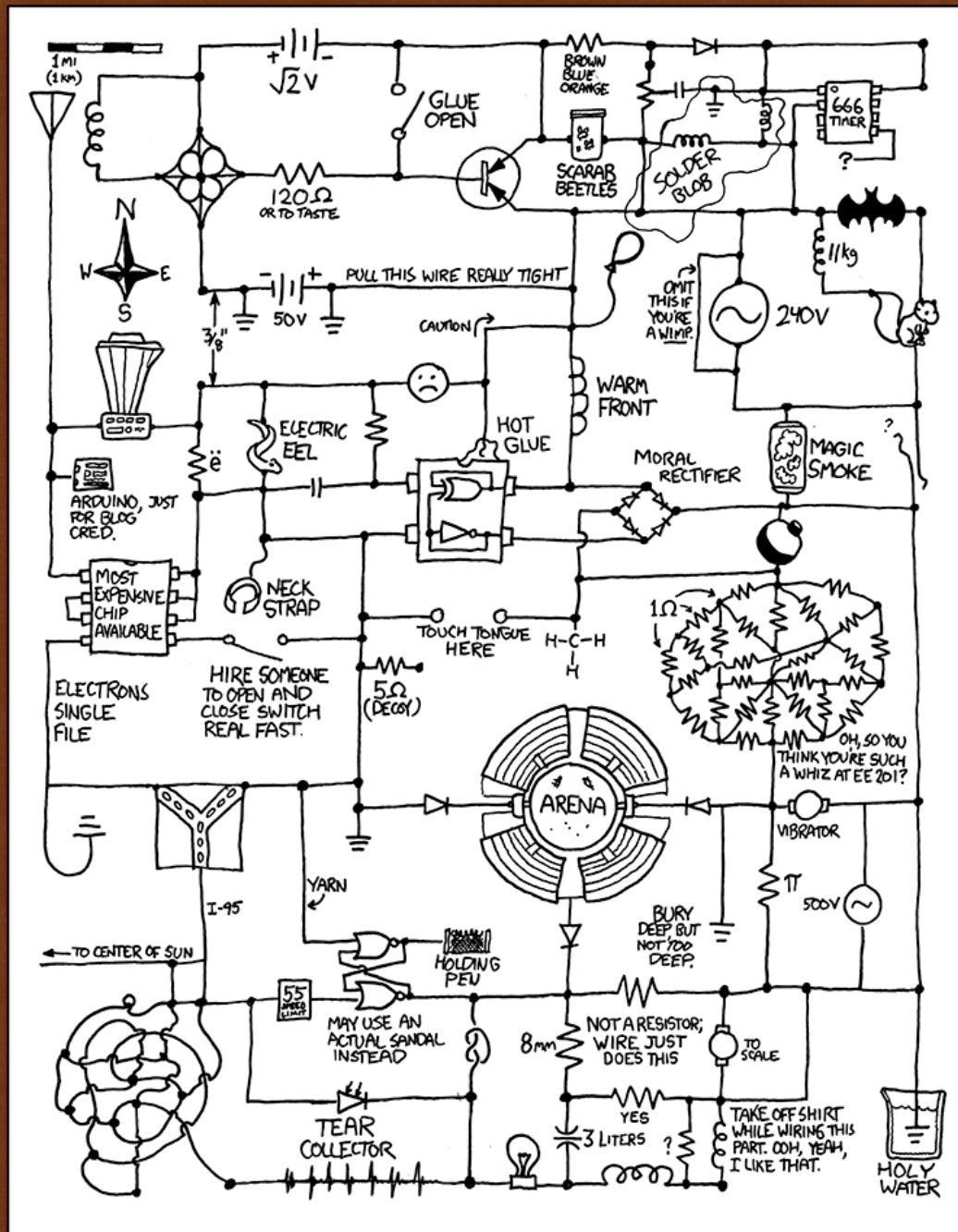


THE BUILDING BLOCKS: SEQUENTIAL CIRCUITS



<https://xkcd.com/730/> - find the latch

LEARNING OUTCOMES

- Selecting values from many (multiplexor)
- Using bits to choose what to do (decoder) The difference between combinational and sequential circuits
- Simple latches
- Implementing registers with simple latches


CONTROL CIRCUITS

- **Control circuits** make decisions, determine order of operations, select data values
- **Multiplexer (mux)** selects one from among many inputs
 - 2^n input lines e.g. 8
 - n selector lines e.g. 3
 - 1 output line - with the output being one of the inputs
- e.g. If we have 4 things to select from we need 2 selector lines
- Each input line corresponds to a unique pattern on selector lines
- That input value is passed to output

2 SOURCE MULTIPLEXOR

$$n = 1$$

FIGURE 4.34

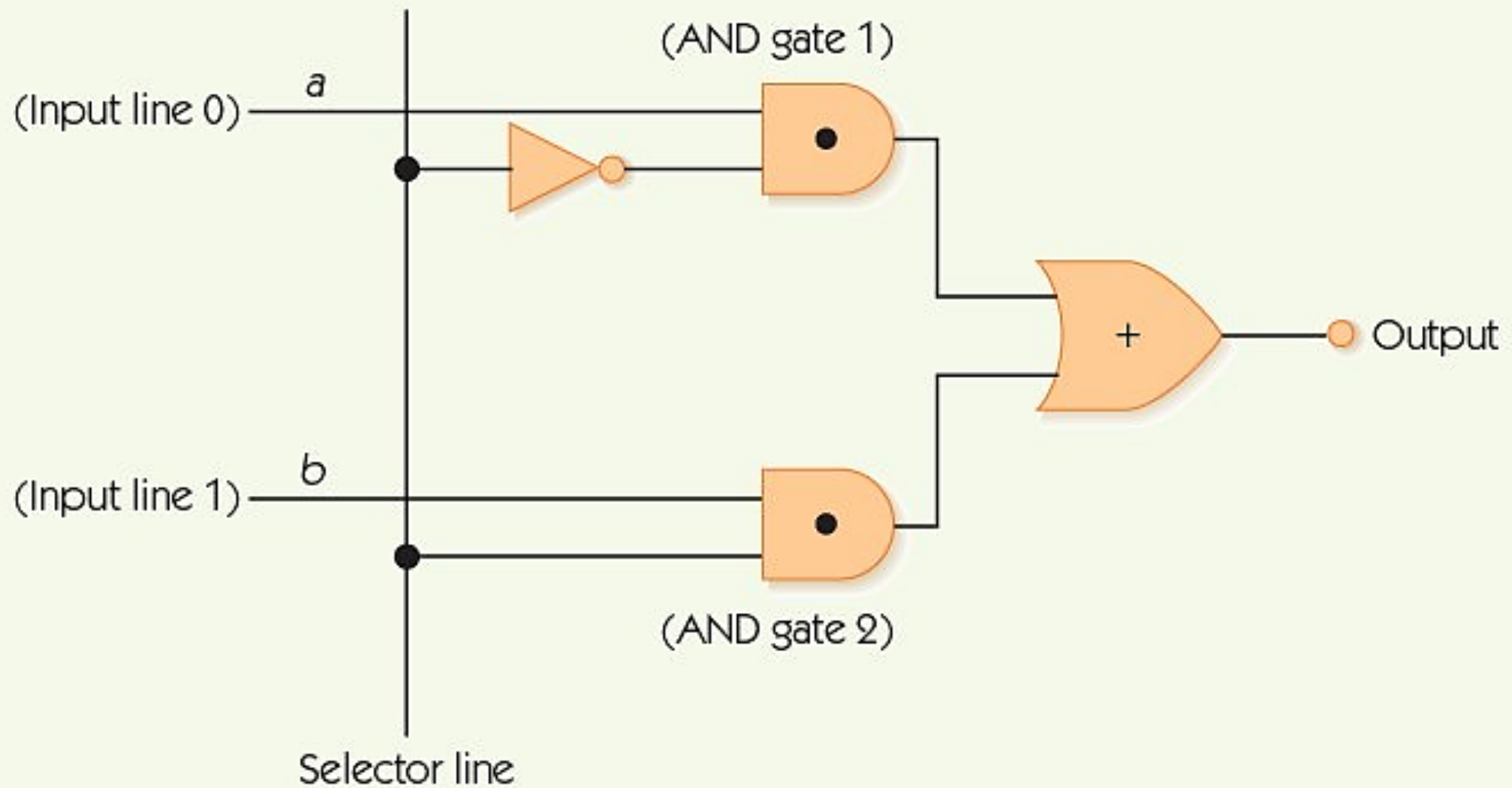


A two-input multiplexor circuit

4 SOURCE MULTIPLEXOR

$$n = 2$$

 - Using the alternative way of drawing circuits it is easier to see how this multiplexor works.




WHAT ABOUT N BIT VALUES?

- The previous 2 slides show 1 of 2 bits or 1 of 4 bits being selected by the multiplexor
- We commonly want to choose 1 of a group of n-bits (e.g. 16 bit values $a_{15}a_{14}...a_2a_1a_0$)
 - to do this we need n multiplexors all connected to the same selector lines
 - each multiplexor passes through one of the bits a_i from the selected value

CHOOSING ONE OF FOUR

FIGURE 4.38

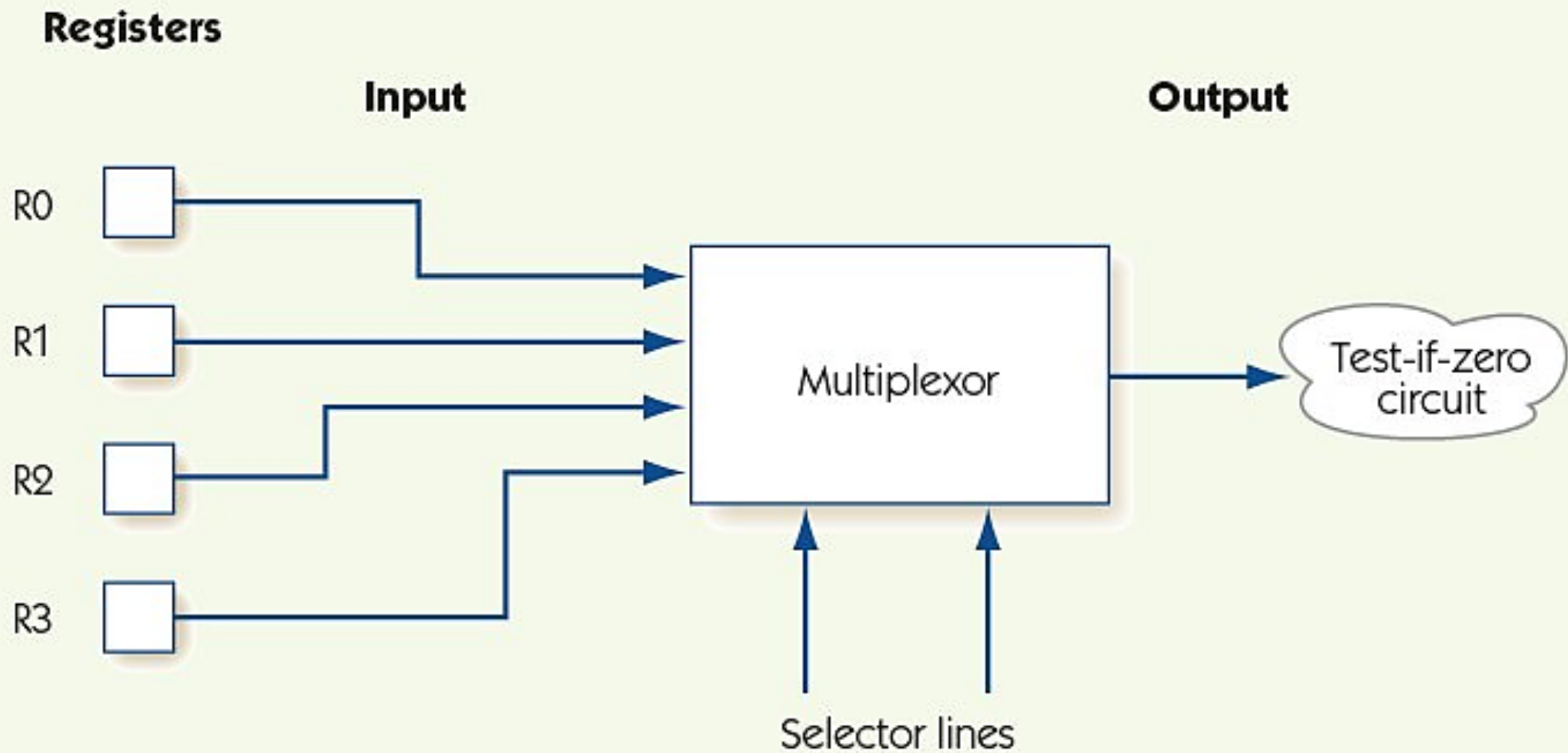

Example of the use of a multiplexor circuit

EXAMPLES OF USING A MULTIPLEXOR

- In a CPU (the processor) multiplexors are used to choose from a variety of inputs e.g. we may have an adder which can add a value from a register or from memory, a multiplexor can choose which one.
- As we will see, CPUs have a special register - the program counter (PC) (which holds a number) - to point to the next instruction to be executed. Normally we add one to the PC to move on to the next instruction. Sometimes we add a different value; a multiplexor could be used to choose the value to add.
- Many data values flow into the multiplexer, only the selected one comes out


DECODER

- **Decoder** sends a signal out to only one output chosen by its input
 - n input lines e.g. 4
 - 2^n output lines e.g. 16
- Sort of like the inverse of a multiplexor, the value coming in on the n input lines chooses one of the 2^n output lines (this line has a value of 1)
- Each output line corresponds to a unique pattern on input lines. In the example a number from 0 to 15 (4 bits) indicates which of the 16 lines get switched on.
- Only the chosen output line produces 1, all others output 0

2 TO 4 DECODER

$$n = 2$$

FIGURE 4.36

 

A 2-to-4 decoder circuit


2 bits determine
which of 4 output
lines is active

EXAMPLES OF USING A DECODER

- Decoder circuit uses
 - To select a single arithmetic instruction, given a code for that instruction (e.g. + is 0, - is 1, \times is 2, \div is 3)
 - Code activates one output line; that line activates corresponding arithmetic circuit
 - More generally we will see we need a way to do different things in our CPUs for different instructions, a decoder is needed to take the bits of an instruction and send signals to other parts of the processor particular to each instruction, e.g. LOAD or STORE or ADD ...

TYPICAL DECODER

FIGURE 4.37

 

Example of the use of a decoder circuit

TWO TYPES OF CIRCUITS

- Combinational Logic Circuit
 - output depends only on the current inputs
 - stateless
 - all the circuits we have seen so far have been combinational
- Sequential Logic Circuit
 - output depends on the sequence of inputs (past and present)
 - stores information (state) from past inputs

COMBINATIONAL VS SEQUENTIAL

- Combinational Circuit
 - always gives the same output for a given set of inputs
 - example: adder always generates same sum and carry if given the same numbers to add regardless of previous inputs
- Sequential Circuit
 - stores information
 - output depends on stored information (state) plus input
 - so a given input might produce different outputs, depending on the stored information
 - example: ticket counter
 - advances when you push the button
 - output depends on previous state
 - useful for building "memory" elements and "state machines"


A SIMPLE LATCH

- A latch holds a value, e.g. the state usually stays either on or off and can be changed from one to the other when required
- Back to Minecraft - <https://www.youtube.com/watch?v=KXScOWZNdBg> and the rest of <https://www.youtube.com/watch?v=OOWaYNf35X4> - 2 minutes 11
- To hold a value we need the circuit to feed back into itself

THE SR LATCH

- A Set Reset latch can be created using NOR or NAND gates we will only look at the NOR gate version.
- The S input means Set the latch i.e. make it 1
- The R input means Reset the latch i.e. make it 0

A	B	A nor B
0	0	1
0	1	0
1	0	0
1	1	0

 


THE SR LATCH TABLE


	S	R	existing out	resulting out
no change	0	0	0	0
Set	1	0	0	1
no change	1	0	1	1
Reset	0	1	1	0
no change	0	1	0	0
no change	0	0	1	1
DON'T	1	1	1	Aaargh!
DON'T	1	1	0	Aaargh!

After a set or reset the S or R reverts to zero, this keeps the value.
So S to one then back to zero makes the output one and
R to one then back to zero makes the output zero.

 
FILL IN THE VALUES AND SEE HOW THEY CHANGE




	S	R	existing out	resulting out
no change	0	0	0	0

 

	S	R	existing out	resulting out
Set	1	0	0	1

 


	S	R	existing out	resulting out
Reset	0	1	1	0

 

REGISTERS

 - A register holds a number of bits - commonly the "word" size of the computer
- We can build a 4 bit register with 4 SR latches
- The latches here are made from OR gates, they are still SR latches
- If D_i is 1 then we store a 1, if 0 we store a 0
- The WE is Write Enable and we set the 4-bit value of the register only when this is 1



PUTTING IT TOGETHER

- We already knew how to encode numbers (and hence any data) into bits. We now know how to create n-bit registers e.g. 16-bit
- If we have two 16-bit registers we can compare corresponding bits from the two registers using the n-bit comparison circuit from the last lecture, i.e. we are comparing two 16-bit numbers
- Similarly we can add or subtract two 16-bit registers by using a 16-bit full adder from lecture 8
- So we can make a simple calculator - we are not going to consider multiplication and division
- The question is what else do we need to add in order to make a computer?